

NEICU MIHAELA


1232A

28.05.2020

A/C  
= FINAL EXAM =


S1  $U_1, U_2$  - op. amp.  $T_1$  has  $V_{BE} = 0.6V$ ,  $V_{CEsat} = 0.2V$ ,  $\beta_{CE} = \infty$ .

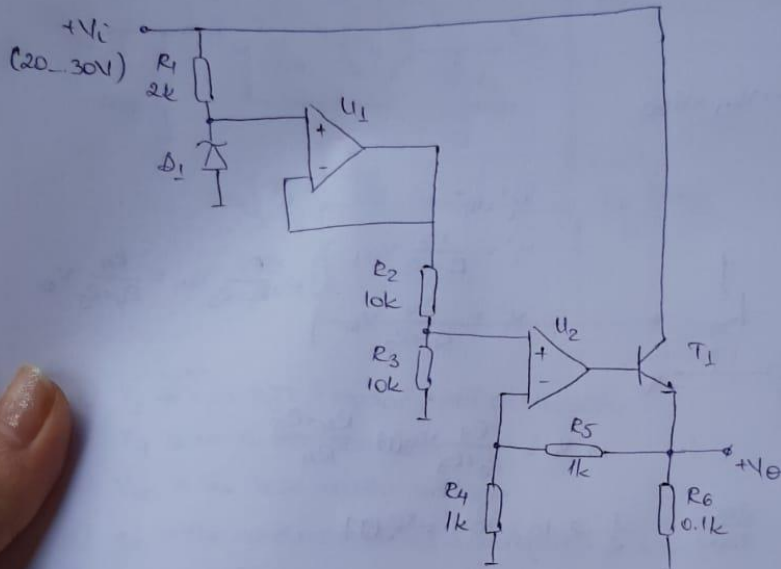$D_1$  is a diode with  $V_{Z0} = 10V$  at  $T = 300K$ ,  $I_{Zmin} = 5mA$ ,  $I_{Zmax} = 50mA$ ,  $r_z = 10\Omega$   
 $\alpha = 1mV/K$




- $D_1$  is a Zener diode
- $R_1$  converts  $V_i$  into current, polarizing the diode  $\Rightarrow$  it acts as a voltage reference for  $U_1$ .
- $U_1$  receives the voltage from  $D_1$  (Zener voltage) and passes it through a voltage divider.
- $U_2$  acts as a source of current at the input of  $T_1$ . (is a voltage buffer)
- $T_1$  provides the output current for the circuit
- $R_2$ - $R_3$  is a voltage divider
- $R_6$  is a pull down resistor

-h)  $V_{\theta} = ?$  (at  $T = 300K$ )

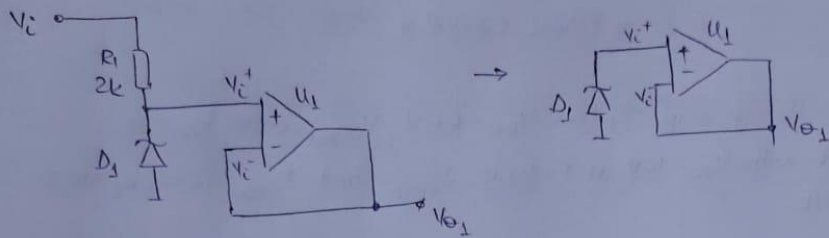
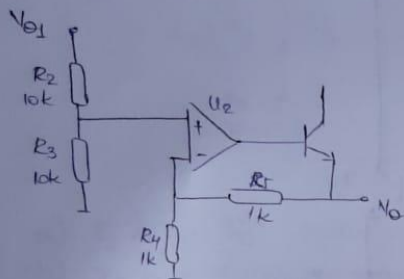
$$\begin{aligned} V_i^+ &= V_i^- \\ V_{Z0} &= V_i^+ \\ V_i^- &= V_{\theta 1} \end{aligned} \quad \left\{ \Rightarrow V_{\theta 1} = V_{Z0} \right.$$



$$\begin{aligned} V_i^+ &= V_i^- \\ V_i^+ &= \frac{R_3}{R_2 + R_3} V_{\theta 1} \\ V_i^- &= \frac{R_4}{R_4 + R_5} V_{\theta} \end{aligned} \quad \left\{ \Rightarrow \frac{R_3}{R_2 + R_3} V_{\theta 1} = \frac{R_4}{R_4 + R_5} V_{\theta} \right.$$

$$\Rightarrow V_{\theta} = \frac{R_3}{R_2 + R_3} V_{Z0} \cdot \frac{R_4 + R_5}{R_4}$$

$$V_{\theta} = \frac{10 \cdot 10^3}{20 \cdot 10^3} \cdot 10 \cdot \frac{2000}{1000} = \frac{1}{2} \cdot 2 \cdot 10 = 10V = \cancel{10.2V}$$

$$\boxed{V_{\theta} = V_{Z0} = 10V} \quad \left\{ \begin{aligned} &\Rightarrow V_{\theta} = V_{Z2}(T) = V_{Z0} + a(T - T_0) \\ &T_0 = 300K \mid \Rightarrow a(T - T_0) = 0 \mid \Rightarrow \\ &T = 300 \end{aligned} \right. \Rightarrow V_{\theta} = V_{Z0}$$

$$\begin{aligned} i) \quad S_{V_{cc}}^{V_{\theta}} &= \frac{V_{cc}}{V_{\theta}} \cdot \frac{dV_{\theta}}{dV_{cc}} = \frac{V_{cc}}{V_{\theta}} \cdot \frac{dV_{Z0}}{dV_{cc}} \\ \frac{dV_{Z0}}{dV_{cc}} &= \frac{r_{Z2}}{R_1} \cdot \frac{1}{1 + \frac{r_{Z2}}{R_1}} \end{aligned} \quad \left\{ \Rightarrow S_{V_{cc}}^{V_{\theta}} = \frac{V_{cc}}{V_{Z0}} \cdot \frac{r_{Z2}}{R_1} \cdot \frac{1}{1 + \frac{r_{Z2}}{R_1}} \right.$$

$$KVL: V_{cc} = V_{ce} + V_{\theta} = 0.2 + 10 = 10.2V$$

$$S_{V_{cc}}^{V_{\theta}} = \frac{10.2}{10} \cdot \frac{10}{2 \cdot 10^{32}} \cdot \frac{1}{1 + \frac{10}{2 \cdot 10^{32}}} = \frac{10.2}{2 \cdot 10^3} \cdot \frac{200}{201} = \frac{20.2}{20 \cdot 201} = 5 \cdot 10^{-3}$$


$$d') V_0(T) = V_z(T)$$

$$V_z(T) = V_{z0} + \alpha(T - T_0) = V_{z0} + \underbrace{1 \cdot 10^{-3}}_{\rightarrow 0} (300 - 300) = V_{z0}$$

S2.

$$T_1, T_2 : \begin{cases} V_{BE} = 0.6V, V_{CEsat} = 0.2V, r_{CE} = 100k\Omega, \beta_F = \beta_R = 100 \end{cases}$$
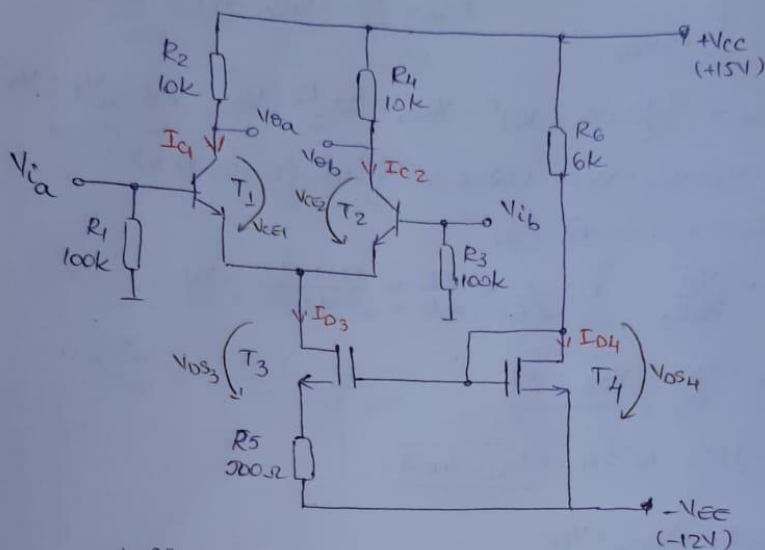
$$T_3, T_4 : \begin{cases} K' = 25\mu A/V^2, \left(\frac{W}{L}\right)_3 = \frac{160}{1}, \left(\frac{W}{L}\right)_4 = \frac{80}{1}, V_T = 1V, \lambda = 3 \cdot 10^{-3}V^{-1} \end{cases}$$




- $T_1$  is an npn BJT (bipolar junction transistor)
- $T_4$  is an N-mos transistor
- $V_{BE}$  is the base-emitter voltage
- $g_m$  is the conductance of a component.  $[g_m] = S$  (Siemens)
- $\beta$  = amplifying factor. It has no measuring unit.
- The amplifier is formed by 2 blocks :
  - the first block ( $T_1, T_2$ ) is a differential amplifier
  - the second block ( $T_3, T_4$ ) is a current mirror

$$K_3 = K' \cdot \left(\frac{W}{L}\right)_3 = 25 \cdot 10^{-6} \cdot 160 = 4 \cdot 10^{-3} = 4mA/V^2$$

$$K_4 = K' \cdot \left(\frac{W}{L}\right)_4 = 25 \cdot 10^{-6} \cdot 80 = 2 \cdot 10^{-3} = 2mA/V^2$$
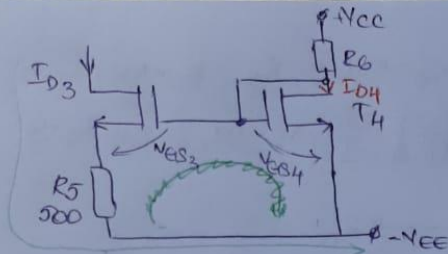
$$V_{CE1} + V_{CE2} = V_{CE3} + V_{CE4} + V_{CE5}$$



$$V_{GS4} = V_{DS4}$$

$$V_{CC} + V_{EE} = I_{D4} \cdot R_6 + V_{DS4} = I_{D4} R_6 + V_{GS4} \Rightarrow$$

$$I_{D4} = \frac{K_4}{2} (V_{GS4} - V_T)^2$$

$$\Rightarrow V_{CC} + V_{EE} = V_{GS4} + \frac{R_6 K_4}{2} (V_{GS4} - V_T)^2 = V_{GS4} + \frac{K_4 R_6}{2} (V_{GS4}^2 - 2V_{GS4} V_T + V_T^2)$$

$$\Delta = 1 + 2K_4 R_6 (V_{CC} + V_{EE} - V_T) = 1 + 2 \cdot 2 \cdot 10^{-5} \cdot 6 \cdot 10^8 \cdot (15 + 12 - 1) \Rightarrow$$

$$\Rightarrow \Delta = 1 + 24 \cdot 26 = 625 \Rightarrow \sqrt{\Delta} = 25$$

$$V_{GS4} = V_T - \frac{1}{K_4 R_6} + \frac{\sqrt{\Delta}}{K_4 R_6} = \frac{12}{2 \cdot 6} - \frac{1}{2 \cdot 6} + \frac{25}{2 \cdot 6} = \frac{12 - 1 + 25}{12} = 3V$$

$$\Rightarrow V_{GS4} = 3V \Rightarrow V_{DS4} = 3V$$

$$I_{D4} = \frac{2 \cdot 10^{-3}}{2} (3 - 1)^2 = 10^{-3} \cdot 4 \Rightarrow I_{D4} = 4 \text{ mA}$$

$$V_{GS3} = V_{DS3} \quad I_{D3} R_5 + V_{DS3} = V_{EE} \Rightarrow V_{EE} = V_{GS3} + \frac{K_3 R_5}{2} (V_{GS3} - V_T)^2$$

$$I_{D3} = \frac{K_3}{2} (V_{GS3} - V_T)^2$$

$$\Delta = 1 + 2K_3 R_5 (V_{EE} - V_T) = 1 + 2 \cdot 4 \cdot 10^{-8} \cdot 0,5 \cdot 10^8 (12 - 1) = 1 + 4 \cdot 11 = 45 \Rightarrow 3\sqrt{5} = \sqrt{\Delta}$$

$$V_{GS3} = V_T - \frac{1}{K_3 R_5} + \frac{\sqrt{\Delta}}{K_3 R_5} = \frac{2}{4 \cdot 0,5} - \frac{1}{4 \cdot 0,5} + \frac{3\sqrt{5}}{4 \cdot 0,5} = \frac{2 - 1 + 3\sqrt{5}}{2} =$$

$$= \frac{1 + 3\sqrt{5}}{2} \approx 3,85 V \Rightarrow V_{DS3} = 3,85 V$$

$$I_{D3} = \frac{4 \cdot 10^{-3}}{2} \left( \frac{1 + 3\sqrt{5}}{2} - 1 \right)^2 = 2 \cdot 10^{-3} \cdot \frac{-1 + 3\sqrt{5}}{2} \approx 10^{-3} \cdot 5,70 \approx 5,7 \text{ mA}$$